

Date:-26/03/2022

Examination Roll NO:- 21312915017

Name of Program:- B.Tech. (Information Tech.
and Mathematical Innovation)

Semester:- 2nd Sem.

Unique Paper Code:- 32861104

Title of the Paper:- Understanding Computer
System Architecture

Solution 2

$$A/q, J_A = Bx + B'y'$$


$$J_B = A'x$$

$$Z = Axy + Bx'y'$$

$$K_A = B'x'y'$$

$$K_B = A + xy'$$

(1) Logic diagram of circuit:

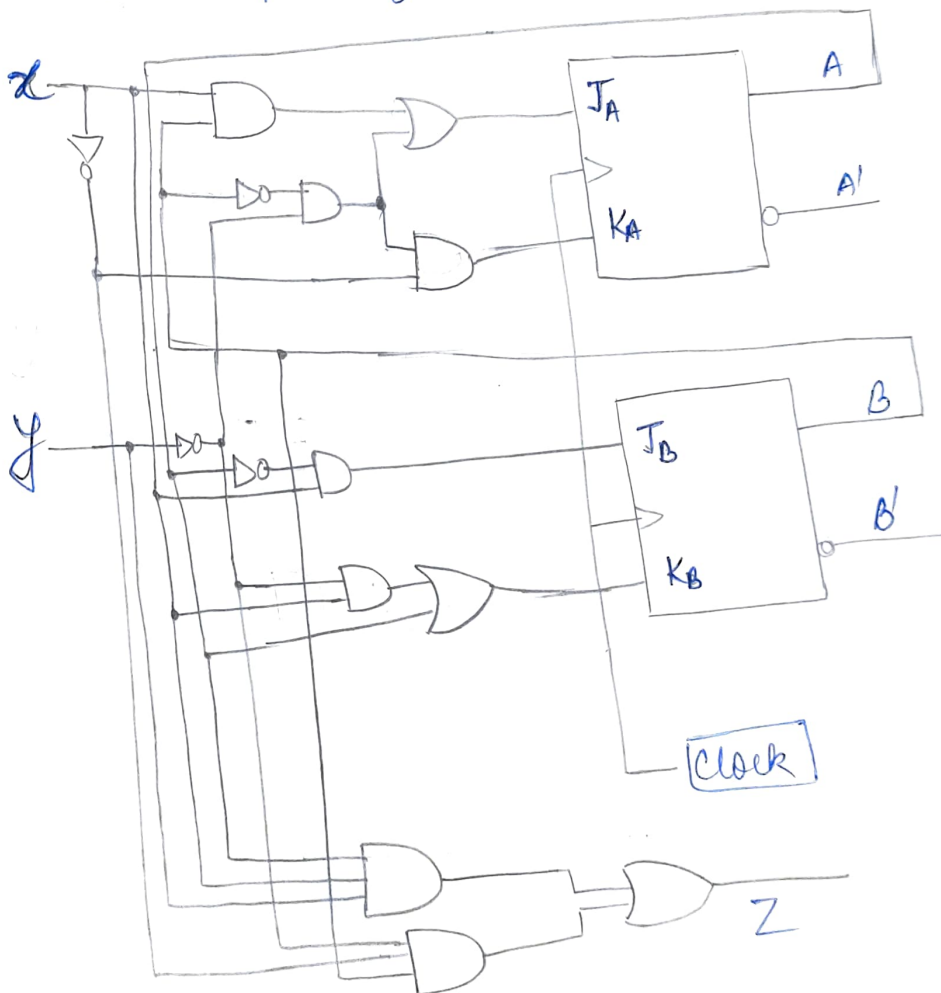

Roll No. :- 21312915017
UPC :- 32861104

(iii) State table.

E/S		I/P		N/S		Flip flops				O/P
A	B	x	y	A'	B'	J _A	K _A	J _B	K _B	Z
0	0	0	0	1	0	1	1	0	0	0
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	1	1	0	1	1	0
0	0	1	1	0	1	0	0	1	0	0
0	1	0	0	0	1	0	0	0	0	1
0	1	0	1	0	1	0	0	0	0	0
0	1	1	0	1	0	1	0	1	1	0
1	0	0	0	0	1	1	0	1	0	0
1	0	0	1	1	0	0	1	0	1	0
1	0	1	0	1	0	0	0	0	1	0
1	0	1	1	1	0	0	0	0	1	0
1	1	0	0	1	0	0	0	0	1	1
1	1	0	1	1	0	0	0	0	1	1
1	1	1	0	1	0	1	0	0	1	0
1	1	1	1	1	0	1	0	0	1	1

iii) Next state eqⁿ.

a) for A

	x'y'	x'y	xy	xy'
A'B'	1	0	0	1
A'B	0	0	1	1
AB	1	1	1	1
AB'	0	1	1	1

~~A(t+1)~~

$$A(t+1) = xy' + xB + AB + yA + A'B'y$$

Roll No.: 21312915017

UPC :- 32861104

3

b) for B

	$x'y$	$x'y'$	xy	xy'
$A'B'$	0	0	1	1
$A'B$	1	1	1	0
AB	0	0	0	0
AB'	0	0	0	0

$$B(t+1) = A'B'x + A'Bx' + A'xy$$